

Университет ИТМО

Кафедра вычислительной техники

**ОТЧЁТ ПО ЛАБОРАТОРНОЙ РАБОТЕ № 2**  
ПО ДИСЦИПЛИНЕ: "СХЕМОТЕХНИКА ЭВМ"  
Вариант №5

Студенты: Куклина М.Д.  
Кириллова А.А.

Преподаватель:

Санкт-Петербург  
2016 г.



# Содержание


1. Цели работы.
2. RTL модель.
3. Временные диаграммы.
4. Листинг.
5. Вывод.

## Цели работы



1. Знакомство с принципами работы последовательных интерфейсов ввода/вывода: I2C, SPI, UART.
2. Изучение основ разработки аппаратных контроллеров периферийных устройств.
3. Изучение основ работы с цифровыми датчиками.

## RTL модель

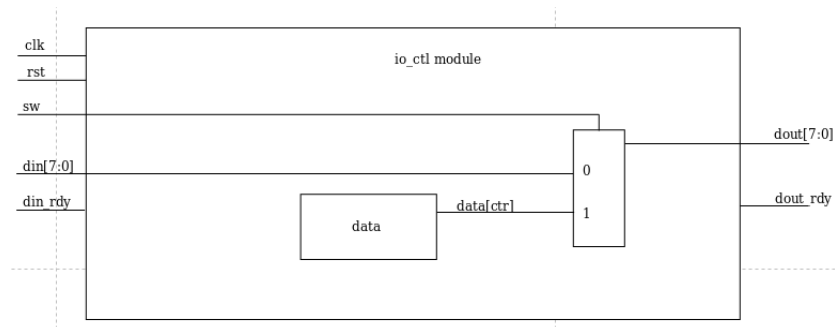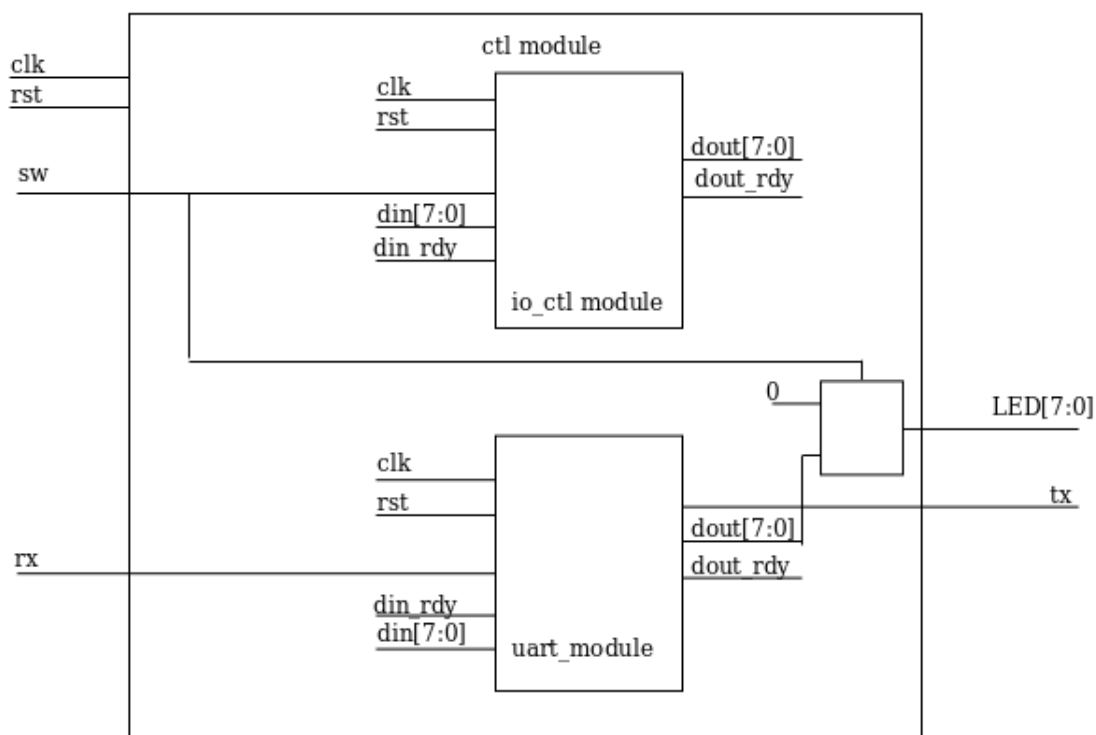

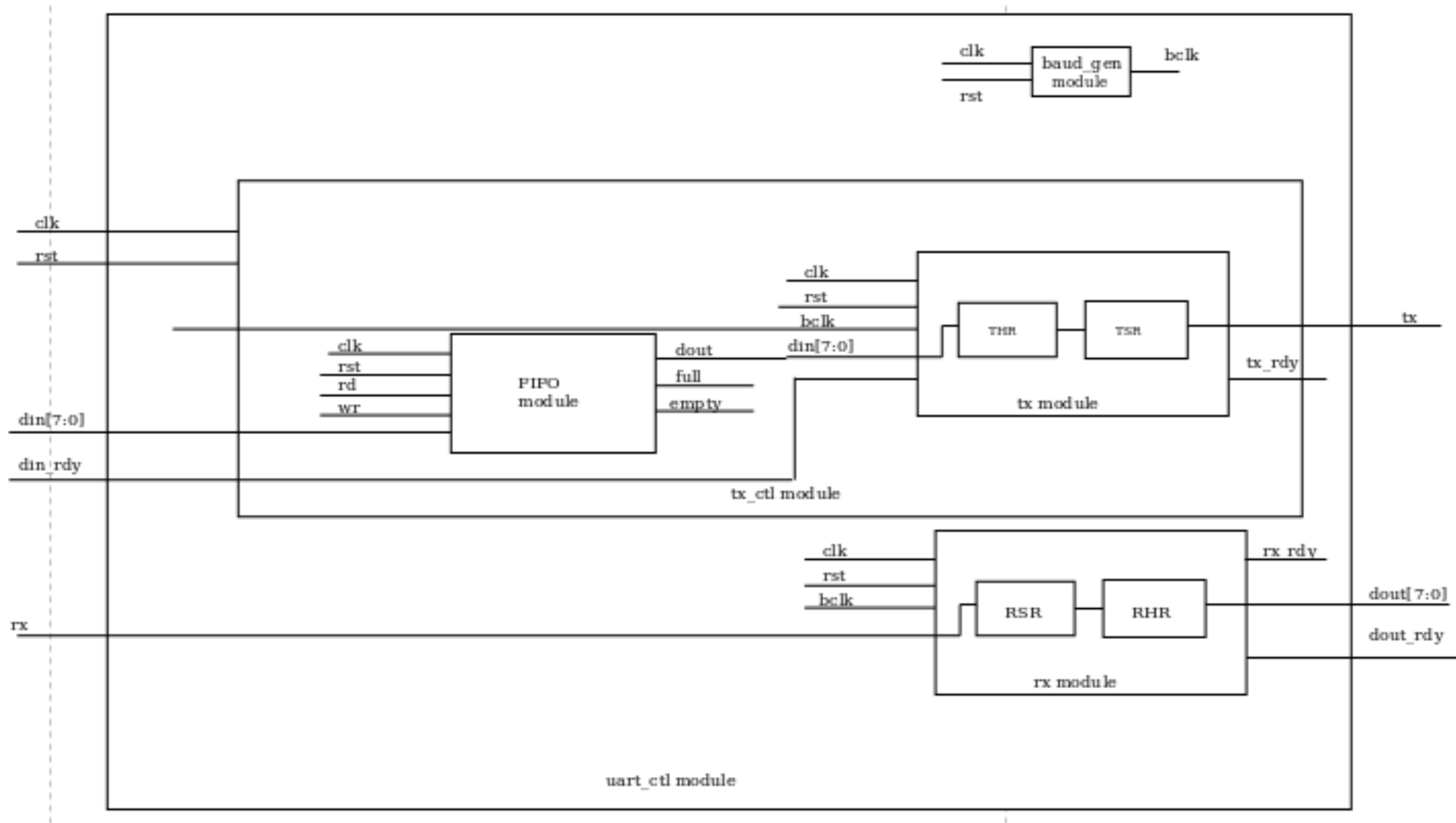

## Временные диаграммы

  

## Листинг

```
1 /* Top module. */
2 module ctl(
3     input          clk ,
4     input          rst ,
5
6     /* UART interface. */
7     input          rx ,
8     output         tx ,
9
10    /* Nexys interface.*/
11    input          sw ,
12    output reg[7:0] led
13 );
14
15 wire [7:0] dout_uart;
16 wire [7:0] dout_io;
17
18 wire dout_io_rdy;
19 wire dour_uart_rdy;
20
21 io_ctl #( 100000000 ) io_ctl(
22     .clk( clk ) ,
23     .rst( rst ) ,
24
25     .sw( sw ) ,
26
27     .din      (dout_uart), /* dout from uart_ctl to io_ctl din */
28     .din_rdy(dout_uart_rdy),
29
30     .dout      (dout_io),
31     .dout_rdy(dout_io_rdy) /* dout_io is ready. */
32 );
33
34 uart_ctl uart_ctl(
35     .clk( clk ) ,
36     .rst( rst ) ,
37
38     .rx      (rx) ,
39     .din      (dout_io) ,
40     .din_rdy(dout_io_rdy) ,
41
42     .tx      (tx) ,
43     .dout      (dout_uart) ,
44     .dout_rdy(dout_uart_rdy)
45 );
46
47 always @(negedge clk)
48     if (rst)
```

```

49         led <= 0;
50         /* SW == 0: echo mode; SW = 1: send mode. */
51         else if ( !sw && dout_uart_rdy)
52             led <= dout_uart;
53
54
55 endmodule

1 module io_ctl #(
2     parameter TIME = 100000000
3 ) (
4     input          clk ,
5     input          rst ,
6     /* SW = 0: echo-mode. SW = 1: send 'Hello world!\r\n'. */
7     input          sw ,
8     /* Data from uart.*/
9     input [7:0]    din ,
10    /* Data to in is ready. */
11    input          din_rdy ,
12    /* Allow read from memory in send mode. */
13    //input        tx_en ,
14    /* Data to uart. */
15    output reg [7:0] dout ,
16    /* Data to out is ready. */
17    output reg      dout_rdy
18 );
19     localparam ECHO_MODE = 0;
20     localparam SEND_MODE = 1;
21
22     reg [7:0] data [14:0];
23     reg [26:0] tm_ctr = 0;
24     reg [3:0] d_ctr = 0;
25     reg was_din_rdy = 0;
26
27
28     /* Have no idea what it is. */
29     wire tx_flag;
30     assign tx_flag = (tm_ctr == TIME) ? 1 :
31                     (( d_ctr == 15 ) || ( d_ctr == 0 )) ? 0 : 1;
32
33     always @( posedge rst ) begin
34         data[0] = "H"; data[1] = "e";   data[2] = "l";
35         data[3] = "l"; data[4] = "o";   data[5] = ",";
36         data[6] = " "; data[7] = "w";   data[8] = "o";
37         data[9] = "r"; data[10] = "l";   data[11] = "d";
38         data[12] = "!";
39         data[13] = 8'h0D; /* \r */
40         data[14] = 8'h0A; /* \n */
41     end
42
43     always @( negedge clk or posedge rst ) begin
44         if( rst )
45             tm_ctr <= 0;
46         else if( sw == SEND_MODE ) begin
47             if( tm_ctr == TIME )
48                 tm_ctr <= 0;
49             else
50                 tm_ctr <= tm_ctr + 1;
51         end
52     end
53
54     always @( posedge clk or posedge rst ) begin
55         if( rst ) begin
56             was_din_rdy <= 0;
57             dout_rdy <= 0;
58             dout <= 0;
59             d_ctr <= 0;
60         end
61         else
62             case( sw )
63                 ECHO_MODE:
64                     begin
65                         if( din_rdy && !was_din_rdy ) begin
66                             was_din_rdy <= din_rdy;
67                             dout <= din;
68                             dout_rdy <= 1;
69                         end
90                     else begin

```

```

71         was_din_rdy <= din_rdy;
72         dout_rdy    <= 0;
73     end
74 end
75 SEND_MODE:
76 begin
77     if( tx_flag ) begin
78         dout_rdy <= 1;
79         dout     <= data[d_ctr];
80         d_ctr    <= d_ctr + 1;
81     end
82     else if( d_ctr == 15 ) begin
83         dout_rdy <= 0;
84         d_ctr    <= 0;
85     end
86 end
87 endcase
88 end
89
90 endmodule

```

```

1 module uart_ctl(
2     input          clk ,
3     input          rst ,
4
5     /* I/O buses. */
6     input          rx ,
7
8     /* Data to send. */
9     input  [7:0]    din ,
10    /* Data to send is ready. */
11    input          din_rdy ,
12
13    output          tx ,
14    /* Received data. */
15    output  [7:0]    dout ,
16    /* Receive ends; data ready. */
17    output          dout_rdy
18    /* Controller ready for transmission. */
19    // output          tx_rdy ,
20    /* Controller ready for reception. */
21    // output          rx_rdy
22 );
23
24 wire      bclk;
25
26 baud_gen  baud_gen(
27     .clk( clk ),
28     .rst( rst ),
29
30     .bclk( bclk )
31 );
32
33 rx_ctl  rx_ctl(
34     .clk  (clk),
35     .rst  (rst),
36
37     .bclk( bclk ),
38     .rx   (rx),
39
40     .dout   (dout),
41     .dout_rdy( dout_rdy ),
42     .rx_rdy  (rx_rdy)
43 );
44
45 tx_ctl  tx_ctl(
46     .clk  (clk),
47     .rst  (rst),
48     .bclk( bclk ),
49
50     .din   (din),
51     .din_rdy( din_rdy ),
52
53     .tx     (tx),
54     .tx_rdy (tx_rdy)
55 );
56
57 endmodule

```

```

1 module rx(
2     input          clk ,
3     input          rst ,
4     input          bclk ,
5     input          rx ,
6
7     output reg[7:0] dout ,
8     output reg      dout_rdy ,
9     output reg      rx_rdy
10 );
11
12 localparam START_BIT = 0;
13 localparam STOP_BIT  = 1;
14
15 localparam IDLE      = 2'd0;
16 localparam START     = 2'd1;
17 localparam STOP      = 2'd2;
18
19
20 reg [7:0] rsr      = 0;
21
22 reg [2:0] d_ctr     = 0;
23 reg [1:0] next_state = 0;
24 reg [1:0] state      = 0;
25
26 reg was_bclk = 0;
27
28
29 always @(negedge clk or posedge rst) begin
30     if (rst)
31         state <= IDLE;
32     else
33         if (!bclk && was_bclk)
34             state <= next_state;
35 end
36
37 always @(posedge clk or posedge rst) begin
38     if (rst) begin
39         next_state <= 0;
40         was_bclk   <= 0;
41         dout_rdy   <= 0;
42         rx_rdy     <= 1;
43         d_ctr      <= 0;
44         rsr        <= 0;
45         dout       <= 0;
46     end
47     else begin
48         if (bclk && !was_bclk) begin
49             was_bclk <= bclk;
50             case (state)
51                 IDLE:
52                     begin
53                         dout_rdy <= 0;
54                         if (START_BIT == rx) begin
55                             next_state <= START;
56                             rx_rdy      <= 0;
57                         end
58                     end
59                 START:
60                     begin
61                         d_ctr <= d_ctr + 1'b1;
62                         rsr   <= rsr << 1;
63                         rsr[0] <= rx;
64                         if (3'd7 == d_ctr) begin
65                             next_state <= STOP;
66                             d_ctr      <= 0;
67                         end
68                     end
69                 STOP:
70                     begin
71                         if (STOP_BIT == rx) begin
72                             dout_rdy <= 1;
73                             dout      <= rsr;
74                         end
75                         next_state <= IDLE;
76                         rx_rdy      <= 0;
77                     end
78             endcase

```

```

79         end
80     else
81         was_bclk <= bclk;
82     end
83 end
84 endmodule

1 module tx_ctl(
2     input          clk ,
3     input          rst ,
4
5     input          bclk ,
6     input [7:0]    din ,
7     input          din_rdy ,
8
9     output         tx ,
10    output         tx_rdy
11 );
12
13    reg wr = 0;
14    reg rd = 0;
15    reg en = 0;
16
17    wire [7:0] fifo_dout;
18
19
20    fifo tx_fifo(
21        .clk( clk ),
22        .rst( rst ),
23
24        .rd ( rd ),
25        .wr ( wr ),
26        /* On next clk data is in memory. */
27        .din( din ),
28
29        .full ( fifo_full ),
30        .empty( fifo_empty ),
31        /* On next clk after the rd signal data is in dout. */
32        .dout ( fifo_dout )
33    );
34
35    tx tx_mod(
36        .clk( clk ),
37        .rst( rst ),
38
39        .bclk( bclk ),
40        /* Data to transmit. */
41        .din( fifo_dout ),
42        /* Data ready to transmit. */
43        .din_rdy( en ),
44        /* TX-pin */
45        .tx( tx ),
46        /* Transmitter is ready ( 1 ), is busy ( 0 ). */
47        .tx_rdy( tx_rdy )
48    );
49
50    /* Read data from buffer to thr for transmission.
51    */
52    always @( posedge clk )
53        if( rst ) begin
54            rd <= 0;
55        end
56        else if( rd ) begin
57            rd <= 0;
58        end
59        /* If fifo isn't empty, tx ready for transmission and no writing
60        * we can read from fifo.
61        * Need tx_rdy to be in untill next transmission.
62        */
63        else if( !fifo_empty && tx_rdy && !wr ) begin
64            rd <= 1;
65        end
66        else
67            rd <= 0;
68
69
70    /* Write data from input to fifo-buffer.*/
71    always @( negedge clk )

```



```

72     if( rst ) begin
73         wr <= 0;
74         en <= 0;
75     end
76     else begin
77         /*
78          * If fifo isn't full, input data is enabled and no reading
79          * we can write to fifo.
80          */
81         if( din_rdy && !fifo_full && !rd )
82             wr <= 1;
83         else
84             wr <= 0;
85
86         if( rd )
87             en <= 1;
88         else
89             en <= 0;
90     end
91 endmodule

1 module tx(
2     input      clk ,
3     input      rst ,
4
5     input      bclk ,
6     input [7:0] din ,
7     input      din_rdy ,
8
9     output reg  tx ,
10    output reg  tx_rdy
11 );
12
13    localparam IDLE      = 3'd0;
14    localparam START     = 3'd1;
15    localparam TRANSMIT  = 3'd2;
16    localparam STOP      = 3'd4;
17    localparam WAIT      = 3'd5;
18
19
20    localparam START_BIT = 1'b0;
21    localparam STOP_BIT  = 1'b1;
22
23    localparam WAIT_TIME_IN_BAUDS = 30;
24
25    reg [7:0] thr      = 0;
26    reg [7:0] tsr      = 0;
27    reg [4:0] wait_time = 0;
28    reg [3:0] dctr      = 0;
29    reg [2:0] next_state = 0;
30    reg [2:0] was_state  = 0;
31    reg [2:0] state     = 0;
32    reg      was_bclk   = 0;
33    reg      tx_en      = 0;
34    reg      rdy        = 0;
35
36    always @(negedge clk or posedge rst)
37        if (rst)
38            state = IDLE;
39        else
40            if (!bclk && was_bclk)
41                state = next_state;
42
43    always @(negedge clk or posedge rst)
44        if (rst) begin
45            tx_en = 0;
46            thr   = 0;
47        end
48        else begin
49            if (din_rdy & !rdy) begin
50                tx_rdy = 0;
51                thr     = din;
52                tx_en   = 1;
53                rdy     = 1;
54            end
55            else
56                if (was_state == IDLE && state == START) begin
57                    tx_en = 0;

```

```

58         end
59         if (was_state == WAIT && state == IDLE) begin
60             tx_rdy = 1;
61             rdy     = 0;
62         end
63     end
64
65
66     always @(posedge clk or posedge rst)
67     if (rst) begin
68         next_state <= IDLE;
69         wait_time  <= 0;
70         was_bclk   <= 0;
71         dctr       <= 0;
72         thr        <= 0;
73         tx_rdy     <= 1;
74         tx         <= 1;
75     end
76     else begin
77         was_state <= state;
78         if (~bclk & !was_bclk) begin
79             was_bclk <= bclk;
80             case( state )
81                 IDLE:
82                     if (tx_en) begin
83                         next_state <= START;
84                         tsr        <= thr;
85                     end
86                 START:
87                     begin
88                         next_state <= TRANSMIT;
89                         tx         <= START_BIT;
90                     end
91                 TRANSMIT:
92                     begin
93                         tx <= tsr[0];
94                         tsr <= tsr >> 1;
95                         dctr <= dctr + 1'b1;
96                         if ( 8 == dctr) begin
97                             next_state <= STOP;
98                             dctr       <= 0;
99                         end
100                     end
101                 STOP:
102                     begin
103                         next_state <= WAIT;
104                         tx         <= STOP_BIT;
105                     end
106                 /* Need to wait between words sending.
107                  * */
108                 WAIT:
109                     begin
110                         wait_time <= wait_time + 1'b1;
111                         if (wait_time == WAIT_TIME_IN_BAUDS) begin
112                             next_state <= IDLE;
113                             wait_time <= 0;
114                         end
115                     end
116                 endcase
117             end
118         else
119             was_bclk <= bclk;
120         end
121     end
122 endmodule

```

```

1 /* Read and write on posedge clk.
2 * Set states of fullness and emptiness by negedge.
3 */
4 module fifo #(
5     parameter DEPTH = 16,
6     parameter CAPACITY = 8
7 ) (
8     input                clk ,
9     input                rst ,
10
11     input                rd ,
12     input                wr ,

```

```

13     input          [CAPACITY-1:0]    din ,
14
15     output          full ,
16     output          empty ,
17     output reg [CAPACITY-1:0]    dout
18 );
19
20     integer i;
21     localparam WRITE = 0;
22     localparam READ  = 1;
23
24     reg [CAPACITY-1:0]    mem [DEPTH-1:0];
25     reg [$clog2(DEPTH)-1:0] raddr    = 0;
26     reg [$clog2(DEPTH)-1:0] waddr    = 0;
27
28     reg state;
29     reg fifo_full;
30     reg fifo_empty;
31
32     assign empty = fifo_empty;
33     assign full  = fifo_full;
34
35     always @( posedge clk or posedge rst ) begin
36         if( rst ) begin
37             for( i = 0; i <= DEPTH-1; i = i + 1 )
38                 mem[i] <= 0;
39             waddr <= 0;
40             raddr <= 0;
41             dout <= 0;
42         end
43         else begin
44             if( wr & !fifo_full ) begin
45                 mem[waddr] <= din;
46                 waddr <= waddr+1'b1;
47                 state <= WRITE;
48             end
49             else if( rd & !empty ) begin
50                 dout <= mem[raddr];
51                 raddr <= raddr + 1'b1;
52                 state <= READ;
53             end
54         end
55     end
56
57     always @( negedge clk or posedge rst )
58     if( rst ) begin
59         fifo_full <= 0;
60         fifo_empty <= 1;
61     end
62     else
63         case( state )
64             READ:
65                 begin
66                     fifo_full <= 0;
67                     if( waddr == raddr )
68                         fifo_empty <= 1;
69                     else
70                         fifo_empty <= 0;
71                 end
72             WRITE:
73                 begin
74                     fifo_empty <= 0;
75                     if( waddr == raddr )
76                         fifo_full <= 1;
77                     else
78                         fifo_full <= 0;
79                 end
80             endcase
81
82 endmodule

```

```

1 /* Generates bauds. */
2 /* For 9600 bps 8N1 — (10417) 9600 bauds. */
3 module baud_gen #(
4     parameter BAUDRATE = 9600
5 )
6 (
7     input          clk ,

```

```

8      input          rst ,
9
10     output reg      bclk
11 );
12     reg [16:0] ctr = BAUDRATE;
13
14     always @( posedge clk ) begin
15         if( rst )
16             ctr <= BAUDRATE;
17
18         if( ctr == BAUDRATE )
19             bclk <= 1;
20         else if( ctr == BAUDRATE/2 )
21             bclk <= 0;
22
23         if( ctr == 0 )
24             ctr <= BAUDRATE;
25         else
26             ctr <= ctr - 16'd1;
27     end
28
29 endmodule

```

## Вывод

В ходы выполнения лабораторной работы были исследованы принципы работы последовательных интерфейсов I/O и в результате разработан универсальный асинхронный интерфейс UART.